



# Chapter I

## Sinusoidal Steady State Analysis

**“Circuit Elements in the Phasor Domain”**




## Objectives

- To introduce phasors and convert the time domain sinusoidal waveform into phasors
- To develop the phasor relationships for the basic circuit elements
- To solve electric circuits in the phasor domain



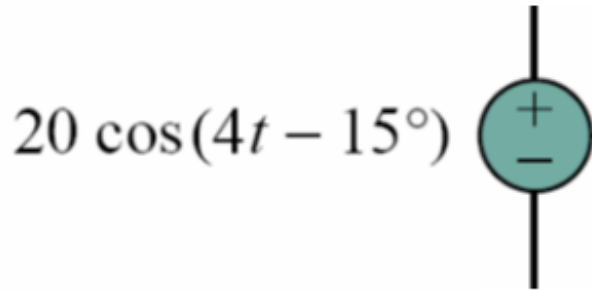
## Phasor Domain Sources

- Convert time domain elements and sources into phasors



Time Domain

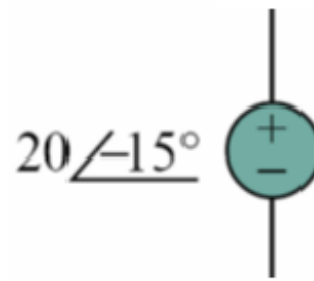

Phasor Domain




# Circuit Elements in Frequency Domain
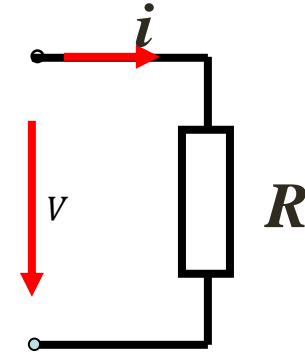
## 1. Resistance


$$i(t) = I_m \cos(\omega t - \psi)$$


$$\begin{aligned} v(t) &= Ri = RI_m \cos(\omega t - \psi) \\ &= V_m \cos(\omega t - \psi) \end{aligned}$$




Then:

$$R = \frac{V_m}{I_m}$$

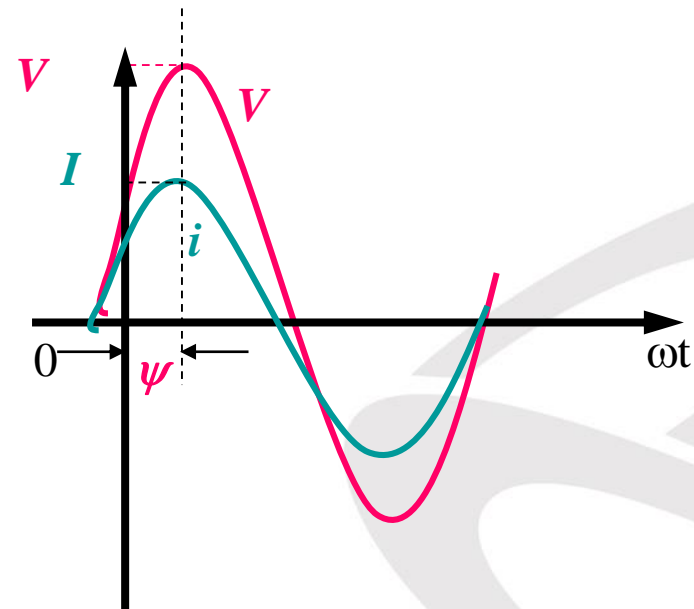


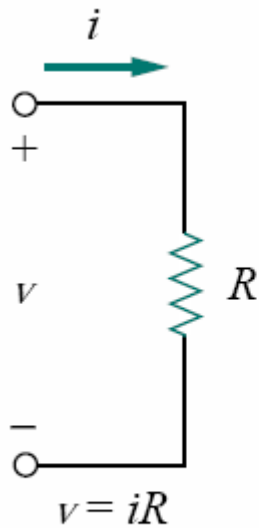

(a)

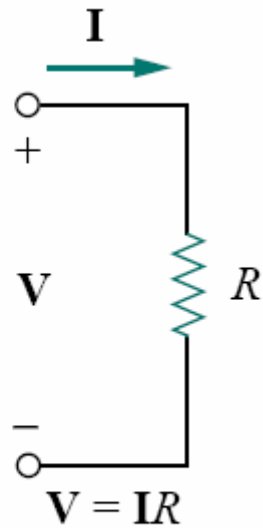

(b)

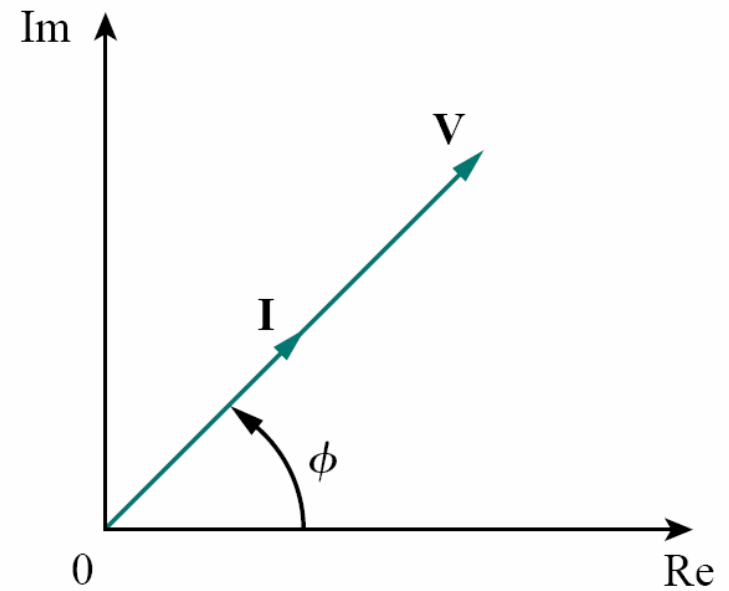


## 2. Inductance


Relationship between voltage and current

$$i(t) = I_m \cos(\omega t - 90) = I_m \sin(\omega t)$$


$$v(t) = L \frac{di}{dt} = \omega L I_m \cos(\omega t) \quad V_m = \omega L I_m$$

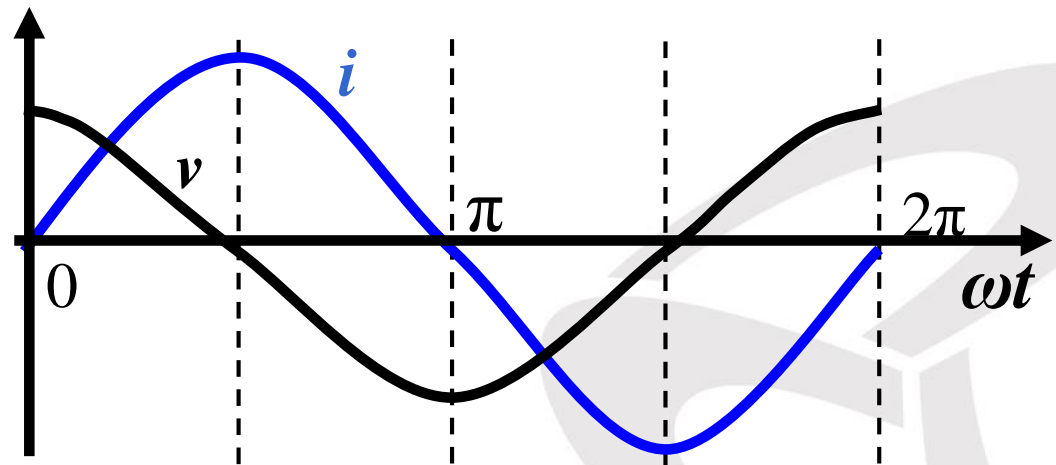$v$  and  $i$  have the same frequency,  $i$  lags  $v$  by  $90^\circ$




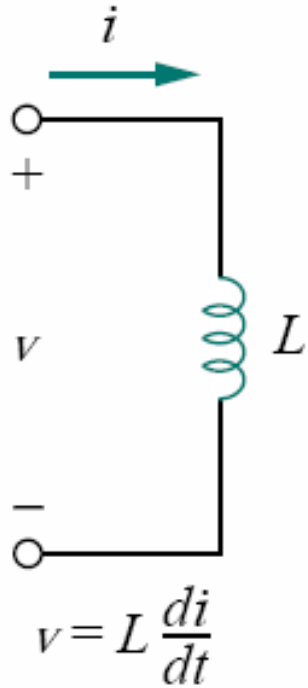

(a)

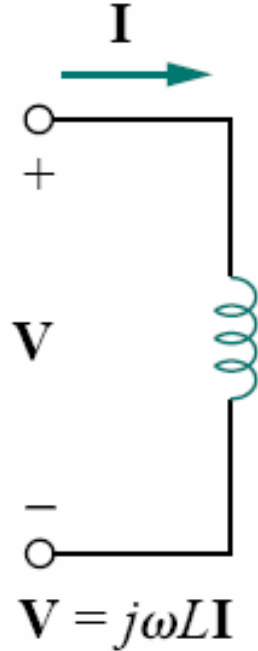

(b)

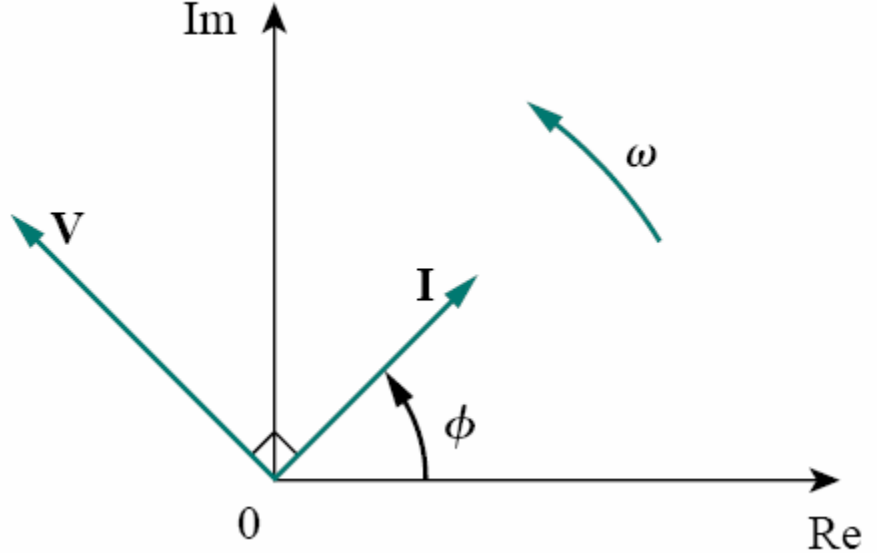

$$X_L = \frac{V_m}{I_m} = \omega L = 2\pi f L$$

$X_L$  is the inductive reactance ( $\Omega$ )



### 3. Capacitors

Relationship between voltage and current

$$v = V_m \sin \omega t$$


$$i = C \frac{dv}{dt} = C \omega V_m \sin(\omega t + 90^\circ) \\ = I_m \sin(\omega t + 90^\circ)$$

$$I_m = \omega C V_m = 2\pi f C V_m$$

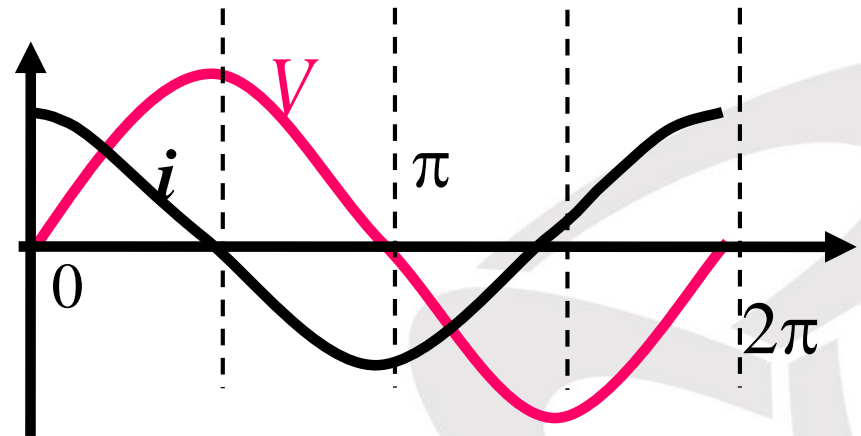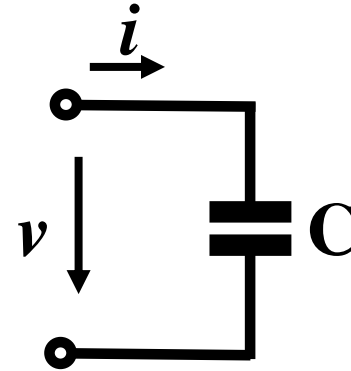


**Current leads voltage by  $90^\circ$**




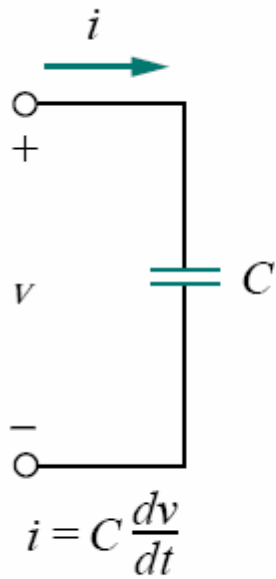

(a)

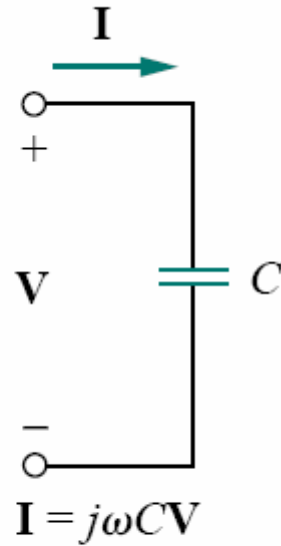

(b)

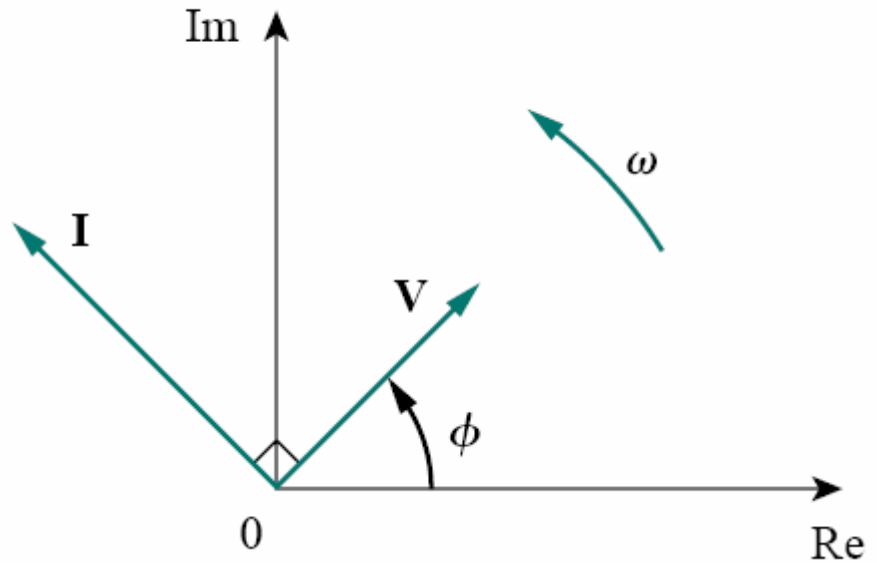

$$X_C = \frac{V_m}{I_m} = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$X_C$  is the capacitive reactance ( $\Omega$ )



## Summary of voltage-current relationship

Element	Time domain	Frequency domain
R	$v = Ri$	$V = RI$
L	$v = L \frac{di}{dt}$	$V = j\omega LI$
C	$i = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$



## Example

The voltage  $v = 12 \cos(60t + 45^\circ)$  is applied to a 0.1-H inductor. Find the steady-state current through the inductor.

### Solution:

For the inductor,  $\mathbf{V} = j\omega L\mathbf{I}$ , where  $\omega = 60$  rad/s and  $\mathbf{V} = 12\angle 45^\circ$  V.  
Hence

$$\mathbf{I} = \frac{\mathbf{V}}{j\omega L} = \frac{12\angle 45^\circ}{j60 \times 0.1} = \frac{12\angle 45^\circ}{6\angle 90^\circ} = 2\angle -45^\circ \text{ A}$$

$$i(t) = 2 \cos(60t - 45^\circ) \text{ A}$$



## Example



If voltage  $v(t) = 6\cos(100t - 30^\circ)$  is applied to a  $50\ \mu\text{F}$  capacitor, calculate the current,  $i(t)$ , through the capacitor.

Answer:  $i(t) = 30 \cos(100t + 60^\circ)\ \text{mA}$


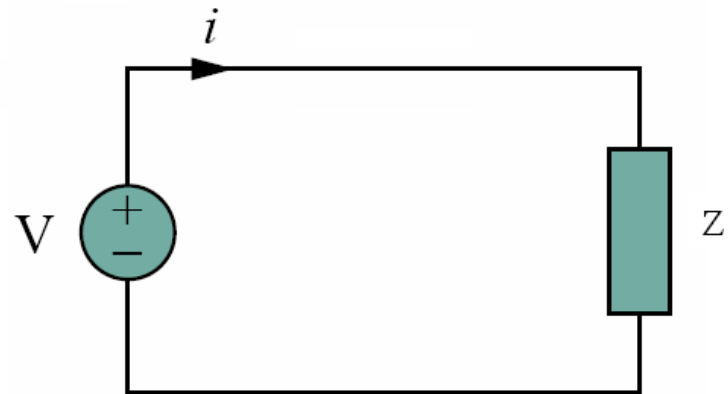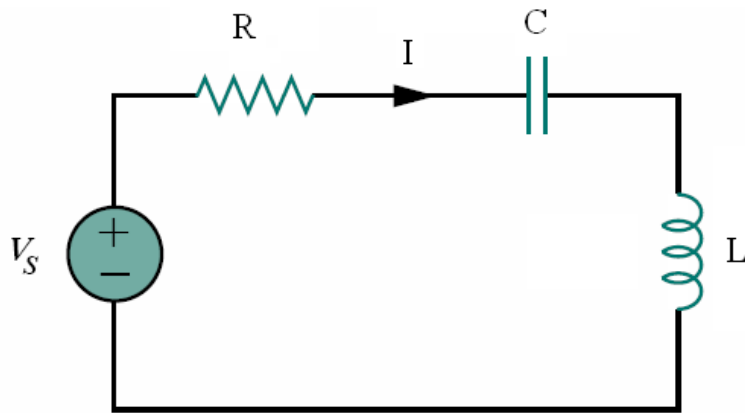
## The Impedance

- Any combination of series and/or parallel resistors, inductors and capacitors form an impedance.
- $Z$  is the impedance where  $Z = R + j\omega L - j / \omega c$





## The admittance

The **admittance**  $\mathbf{Y}$  is the reciprocal of impedance, measured in siemens (S).

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} \quad \text{or} \quad \mathbf{V} = \mathbf{Z}\mathbf{I}$$

$$\mathbf{Y} = \frac{1}{\mathbf{Z}} = \frac{\mathbf{I}}{\mathbf{V}}$$

$$\mathbf{Z} = R \pm jX = |\mathbf{Z}|/\underline{\theta}$$

$$\mathbf{Y} = G + jB$$

$$G + jB = \frac{1}{R + jX}$$


$$G + jB = \frac{1}{R + jX} \cdot \frac{R - jX}{R - jX} = \frac{R - jX}{R^2 + X^2}$$

Equating the real and imaginary parts gives

$$G = \frac{R}{R^2 + X^2}, \quad B = -\frac{X}{R^2 + X^2}$$


## Series and parallel Impedances

### Series

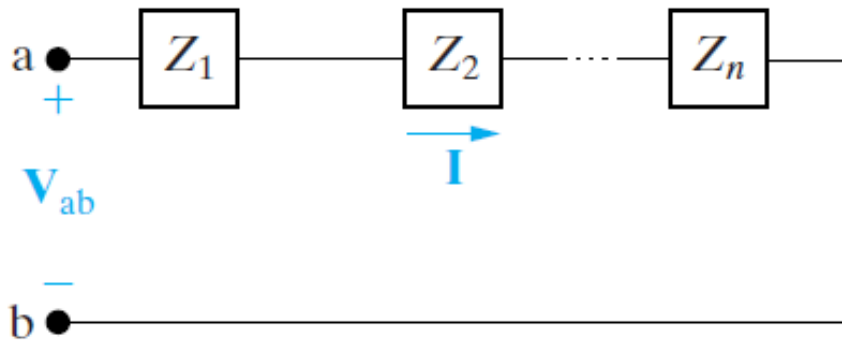

$$Z_{ab} = \frac{V_{ab}}{I} = Z_1 + Z_2 + \dots + Z_n.$$

### parallel

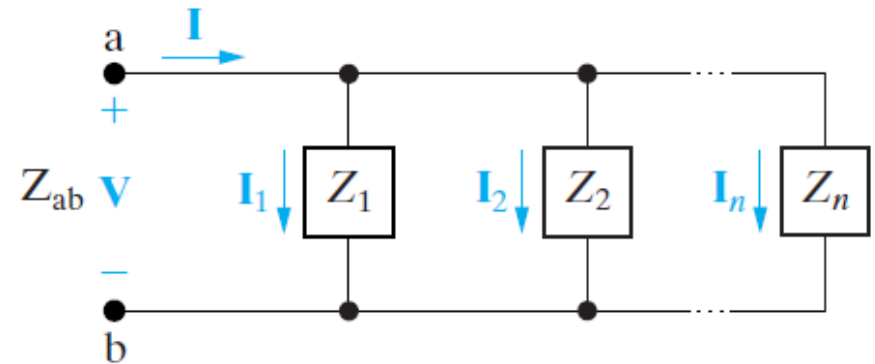

$$I = I_1 + I_2 + \dots + I_n,$$

$$\frac{V}{Z_{ab}} = \frac{V}{Z_1} + \frac{V}{Z_2} + \dots + \frac{V}{Z_n}.$$

$$Y = \frac{1}{Z} = G + jB$$

$$Y_{ab} = Y_1 + Y_2 + \dots + Y_n.$$



## Kirchhoff's Laws in the Frequency Domain

- Both KVL and KCL are hold in the phasor domain or more commonly called frequency domain.
- Moreover, the variables to be handled are phasors, which are complex numbers.
- Series and parallel combinations are the same as in DC circuits analysis.
- All the mathematical operations involved are now in complex domain.





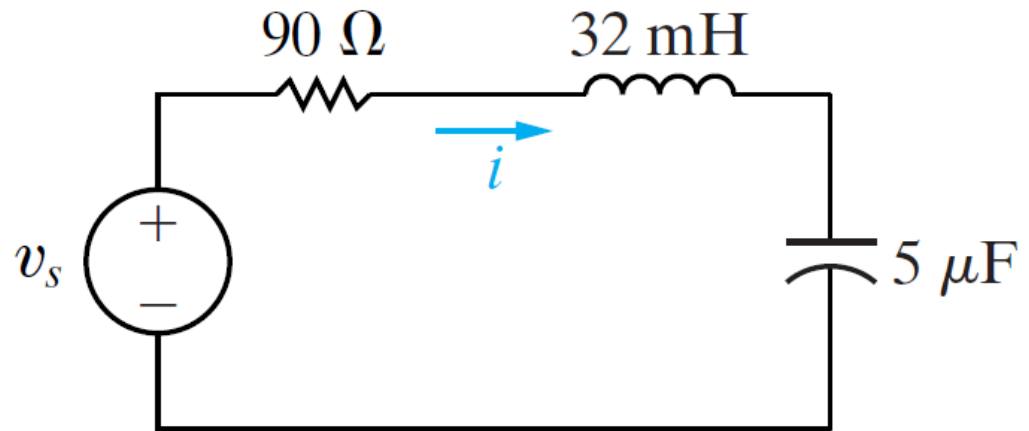
## Example

Refer to Figure below, determine the time domain expression for the steady state current.

$$v_s \text{ is } 750 \cos(5000t + 30^\circ) \text{ V}$$




## Answer

$$\mathbf{I} = \frac{750 \angle 30^\circ}{150 \angle 53.13^\circ} = 5 \angle -23.13^\circ \text{ A.} \quad i = 5 \cos(5000t - 23.13^\circ) \text{ A.}$$

## Example


$$i_s = 8 \cos 200,000t \text{ A}$$

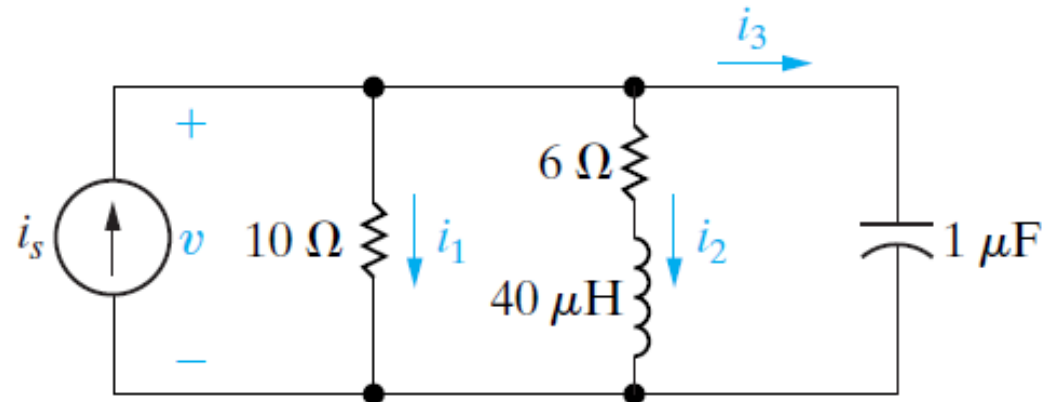

Find the steady-state expressions for  $v$ ,  $i_1$ ,  $i_2$
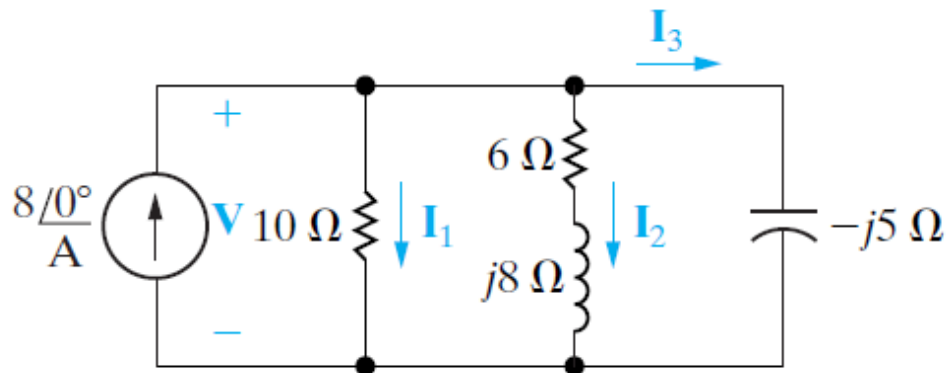
## Solution

**Step 1:** Construct the phasor domain circuit



**Step 2:** Apply circuit analysis technique

$$Y = Y_1 + Y_2 + Y_3$$

$$= 0.16 + j0.12$$

$$= 0.2 \angle 36.87^\circ \text{ S.}$$


$$Z = \frac{1}{Y} = 5 \angle -36.87^\circ \Omega$$

$$\mathbf{V} = \mathbf{ZI} = 40 \angle -36.87^\circ \text{ V.}$$


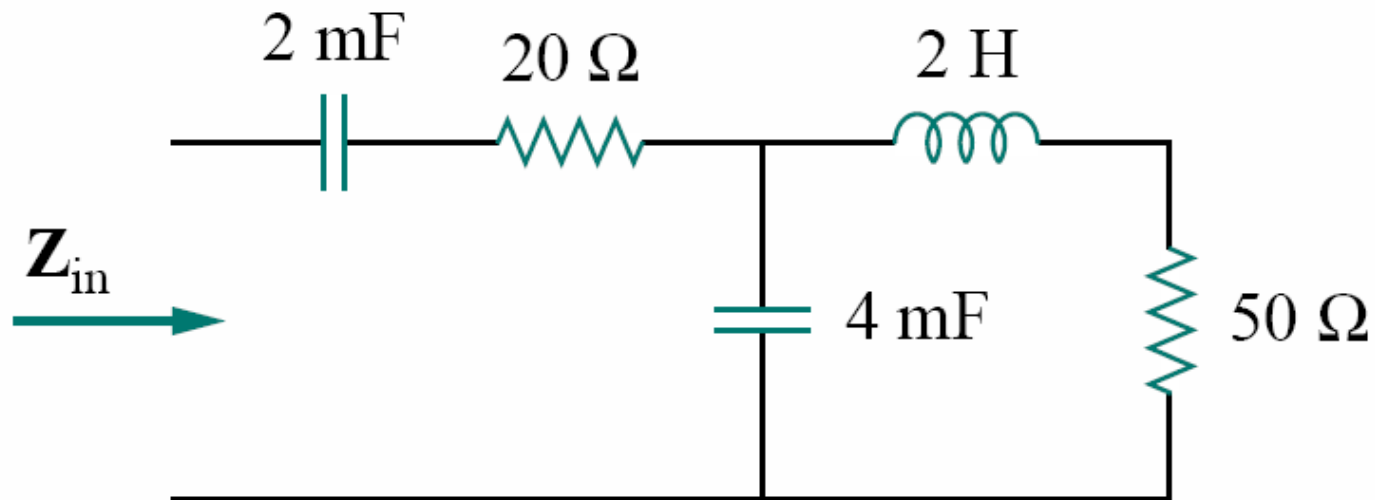
## Impedance Combinations

Determine the input impedance of the circuit in figure below at  $\omega = 10$  rad/s.



Answer:  $Z_{in} = 32.38 - j73.76$